

This question paper contains 3 printed pages]

**R—360—2017**

**FACULTY OF SCIENCE**

**B.Sc. (Second Year) (Third Semester) EXAMINATION**

**APRIL/MAY, 2017**

**COMPUTER SCIENCE**

**Paper VI**

**(Digital Electronics and 8085 Microprocessor)**

**(MCQ & Theory)**

**(Saturday, 6-5-2017)**

**Time : 2.00 p.m. to 4.00 p.m.**

*Time—2 Hours*

*Maximum Marks—40*

*N.B. :— (i) All questions are compulsory.*

*(ii) Figures to the right indicate full marks.*

**MCQ**

1. Multiple Choice Questions : 10

(i) ..... logic gates are called basic gates.

(a) NAND, NOR (b) AND, OR, NOT

(c) Ex-OR, Ex-NOR (d) All of these

(ii)  $Y = A \oplus B$  is a logic equation of ..... gate.

(a) OR (b) AND

(c) Ex-OR (d) All of these

(iii) Maximum possible cells in four variable K-map are .....

(a) Two (b) Four

(c) Eight (d) Sixteen

P.T.O.

- (iv)  $\overline{A \cdot B} = \dots\dots\dots$  in boolean Algebra.
- (a)  $\bar{A} + \bar{B}$  (b)  $\bar{A} - \bar{B}$
- (c)  $AB$  (d) All of these
- (v) T-FF is called  $\dots\dots\dots$  flip-flop.
- (a) Temporary flip-flop (b) Toggle flip-flop
- (c) Time flip-flop (d) All of these
- (vi)  $A + 1 = \dots\dots\dots$  in boolean Algebra.
- (a) 0 (b) 1
- (c) A (d) All of these
- (vii) Word size of 8085 microprocessor is  $\dots\dots\dots$  bit.
- (a) Eight (b) Sixteen
- (c) Four (d) None of these
- (viii) LDA address instruction is  $\dots\dots\dots$  byte.
- (a) One (b) Two
- (c) Three (d) All of these
- (ix) 8085 microprocessor is  $\dots\dots\dots$  pin IC.
- (a) Eight (b) Sixteen
- (c) Forty (d) None of these
- (x) Program counter is a  $\dots\dots\dots$  bit register.
- (a) Eight (b) Sixteen
- (c) Twenty (d) None of these

### Theory

2. (a) What is logic gate ? Explain AND, OR, NOT logic gates in detail.

*Or*

- (b) Reduce the following equation using K-map : 5  

$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}D + ABCD.$$
- (c) Explain addition, subtraction, multiplication laws in Boolean Algebra. 5
3. (a) Explain two variable, three variable and four variable K-map with example. 10
- Or*
- (b) Explain SRFF in detail. 5
- (c) Write a program for addition of two 8-bit numbers in 8085 microprocessor. 5
4. (a) Explain pin diagram of 8085 microprocessor. 10
- Or*
- (b) Explain any *four* logical instructions of 8085 microprocessor. 5
- (c) Explain flag registers of 8085 microprocessor. 5