

This question paper contains 3 printed pages]

AO—355—2018

FACULTY OF SCIENCE

B.Sc. (Third Semester) EXAMINATION

MARCH/APRIL, 2018

COMPUTER SCIENCE

Paper VI

(Digital Electronics and 8085 Microprocessor)

(MCQ+Theory)

(Saturday, 28-4-2018)

Time : 2.00 p.m. to 4.00 p.m.

Time—2 Hours

Maximum Marks—40

(MCQ)

1. (i) The output of an OR gate of LOW when
- (A) any input is LOW (B) any input is HIGH
(C) all inputs are LOW (D) all inputs are HIGH
- (ii) The Boolean expression for a 3-input AND gate is
- (A) $X = AB$ (B) $X = ABC$
(C) $X = A + B + C$ (D) $X = AB + C$
- (iii) How many cells are required in K-map for 3 variables ?
- (A) 1 (B) 2
(C) 4 (D) 8
- (iv) The simplest equation which implements the K-map shown below is :

	\bar{C}	C
$\bar{A}\bar{B}$	0	0
$\bar{A}B$	1	1
AB	1	1
$A\bar{B}$	0	1

- (A) $X = AC + B$ (B) $X = A\bar{B}$
(C) $AB\bar{C} + ABC + A\bar{B}C$ (D) $AB + \bar{A}B$

P.T.O.

- (v) A J-K flip-flop is in a 'no-change' condition when
- (A) $J = 1, K = 1$ (B) $J = 1, K = 0$
(C) $J = 0, K = 1$ (D) $J = 0, K = 0$
- (vi) Popular application flip-flop are ?
- (A) Counters
(B) Shift registers
(C) Transfer registers
(D) All of the above
- (vii) Register is a :
- (A) Set of capacitor used to register input instructions in a digital computer
(B) Set of paper tapes and cards put in a file
(C) Temporary storage unit within the CPU having dedicated or general purpose use
(D) Part of the auxiliary memory
- (viii) A simple flip-flop :
- (A) is a 2 bit memory
(B) is a 1 bit memory
(C) is a four state device
(D) has nothing to do with memory
- (ix) The communication line between the CPU, memory and peripherals is called a
- (A) Bus (B) Line
(C) Media (D) None of these
- (x) The 8085 microprocessor uses power supply.
- (A) + 5 V (B) - 5 V
(C) + 12 V (D) - 12 V

(Theory)

2. Explain the universal properties of NAND and NOR operation with truth table and circuit diagram. 10

Or

- (a) Explain the two variable Karnaugh map method with example. 5
 (b) Explain don't care condition. 5
3. Draw the circuit diagram of the Ripple counter and explain its operation. Give its timing diagram. 10

Or

- (a) Explain the concept of RS flip-flop. 5
 (b) Explain the concept of 1-bit memory cell. 5
4. Explain the architecture of 8085 microprocessor. 10

Or

- (a) What is microprocessor ? Explain in detail. 5
 (b) Explain microprocessor operation. 5