

This question paper contains 2 printed pages]

BF—98—2016

FACULTY OF SCIENCE

B.Sc. (Third Year) (Sixth Semester) EXAMINATION

OCTOBER/NOVEMBER, 2016

(New Course)

PHYSICS

Paper XV (Phy-305)

(Digital and Communication Electronics)

(Monday, 24-10-2016)

Time : 10.00 a.m. to 12.00 noon

Time—2 Hours

Maximum Marks—40

N.B. :— (i) All questions are compulsory.

(ii) All questions carry equal marks.

1. Attempt any *four* : 8

- (a) What do you mean by wire and wireless communication ?
- (b) Define base band signal.
- (c) Define sensitivity, selectivity and fidelity of AM receiver.
- (d) Define AM and FM.
- (e) State distributive laws.
- (f) State AND laws.
- (g) Draw the circuit diagram of EX-NOR gate using basic gates.
- (h) Draw the truth table and logic symbols of OR gate and NOR gate.

2. Attempt any *two* : 8

- (a) Perform the following conversions :
 $(654)_8 = (?)_2$
 $(498)_{10} = (?)_2$
 $(ABC)_{16} = (?)_2$
 $(1001110)_2 = (?)_8$
- (b) State and explain De Morgan's theorems.
- (c) Explain the frequency spectrum of amplitude modulated wave with neat diagram.

P.T.O.

3. Attempt any *two* : 8
- (a) Construct OR, AND, NOT and NAND gate using NOR gate.
- (b) Draw K-map, for the following expression :
- $$Y = \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D} + \bar{A}B\bar{C}D$$
- (c) Draw the block diagram of superheterodyne receiver and explain function of each block.
4. Attempt any *one* : 8
- (a) Define modulation index and deviation ratio for FM. Obtain an expression for frequency modulated wave.
- Or*
- (b) Why do you need modulation ?
5. Write short notes on any *two* : 8
- (a) Universal properties of NAND gate
- (b) Linear diode detector
- (c) Basic communication system
- (d) TRF receiver.