

This question paper contains 2 printed pages]

SA—17—2025

FACULTY OF SCIENCE

B.Sc. (Third Year) (Sixth Semester) EXAMINATION

APRIL/MAY, 2025

PHYSICS

(Digital and Communication Electronics-XV)

(Friday, 11-4-2025)

Time : 10.00 a.m. to 12.00 noon

Time—2 Hours

Maximum Marks—40

N.B. :- (i) All questions are compulsory.

(ii) Figures to the right indicate full marks.

(iii) Use of non-programmable calculator is allowed.

1. What is gate ? Explain AND, OR and NOT gates with their logic symbols, Boolean equations and truth tables. 15

Or

(x) Carry out the following arithmetic : 8

(a) $(0110111)_2 + (001111)_2$

(b) $(10111)_2 - (01101)_2$

(c) $(110001)_2 \times (1110101)_2$

(d) $(1110101)_2 \div (1001)_2$

(y) Discuss excess 3 code and gray code. 7

P.T.O.

2. What are the types of modulations ? Derive an expression for frequency modulated wave. 15

Or

- (x) Draw block diagram of basic communication system. Explain each block. 8
- (y) Explain characteristics of radio receiver : 7
- (i) Selectivity
 - (ii) Sensitivity
 - (iii) Fidelity.
3. Write short notes on any *two* : 10
- (a) Universal properties of NAND gate
 - (b) De-Morgan's theorems
 - (c) Essential elements of A.M. transmitter
 - (d) Linear diode A.M. detector.